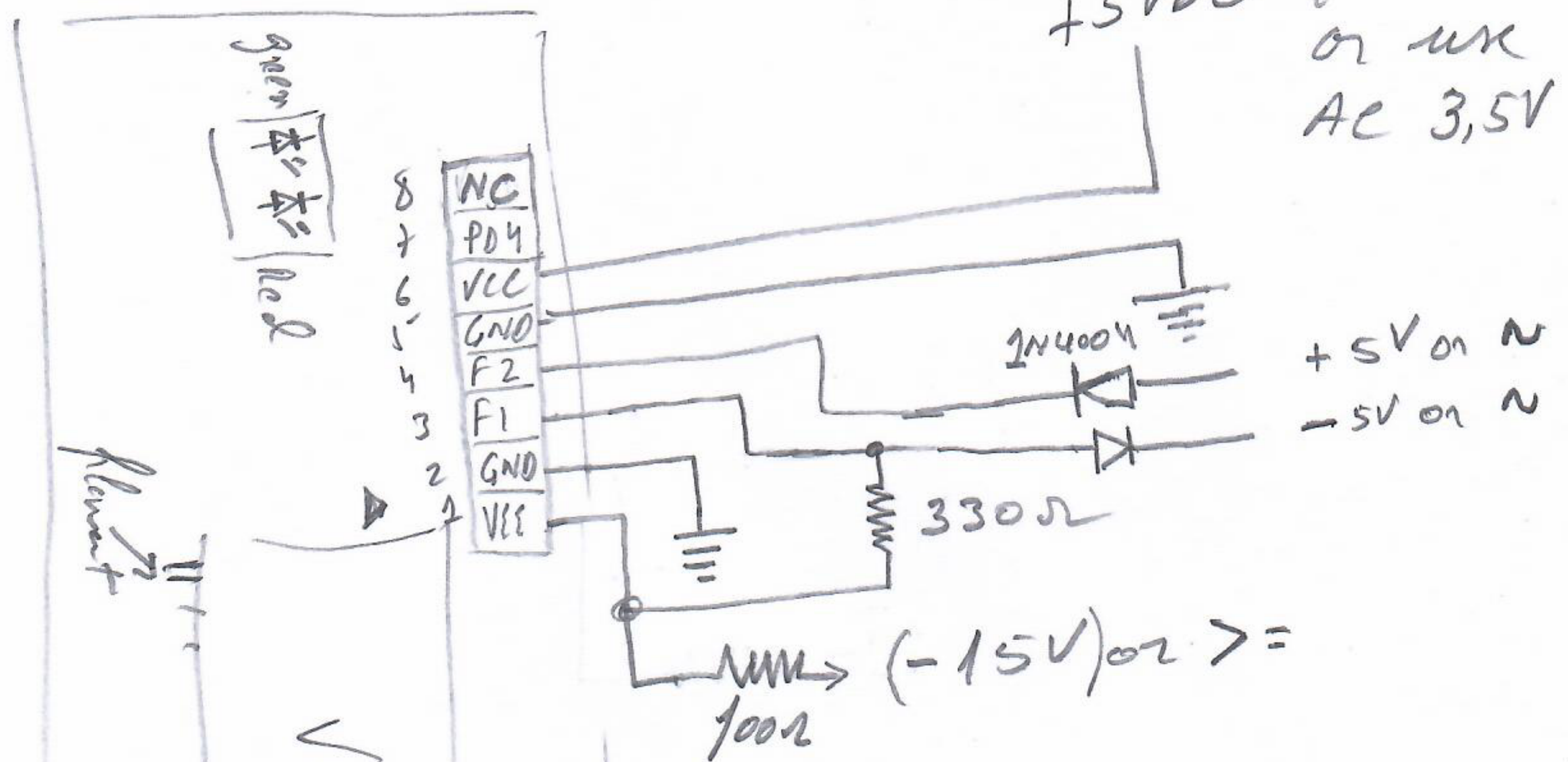



Each diode 1N4004 drop 0,7V
 $2 \cdot 0,7 = 1,4V$ $5 - 1,4V = 3,6V$ to
 +5VDC filaments
 or UK
 AC 3,5V



Note: Necessary 3 independent sources !!! Also is possible use only 2 can use a converter DC/DC like B0524S because is a isolated converter.

See my channel "how power up a VFD"

Any question feel free, OK.

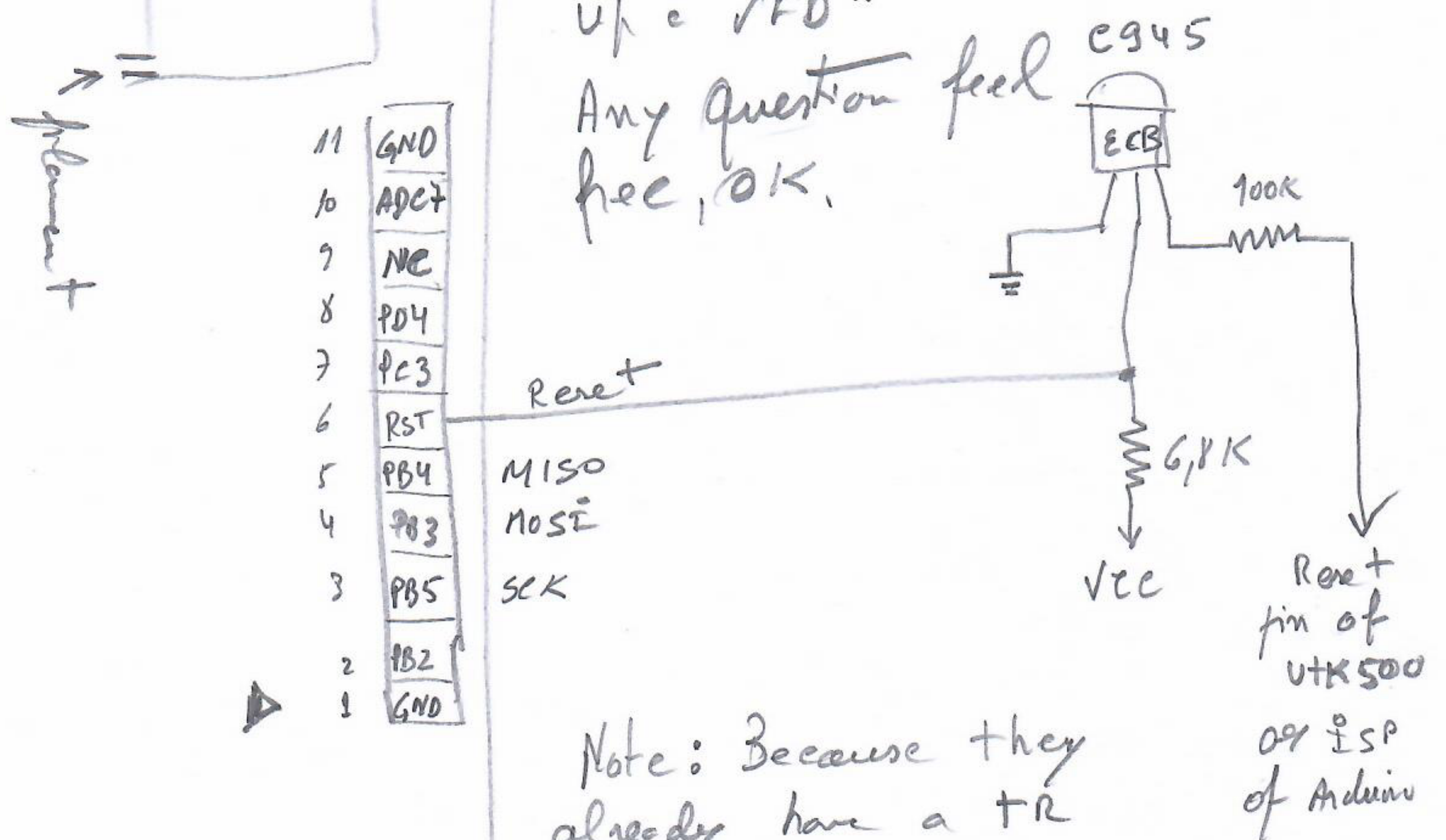

Note: Because they already have a TR in the board are necessary do again the insertion of signal of RST I'm using the C945 to do it.